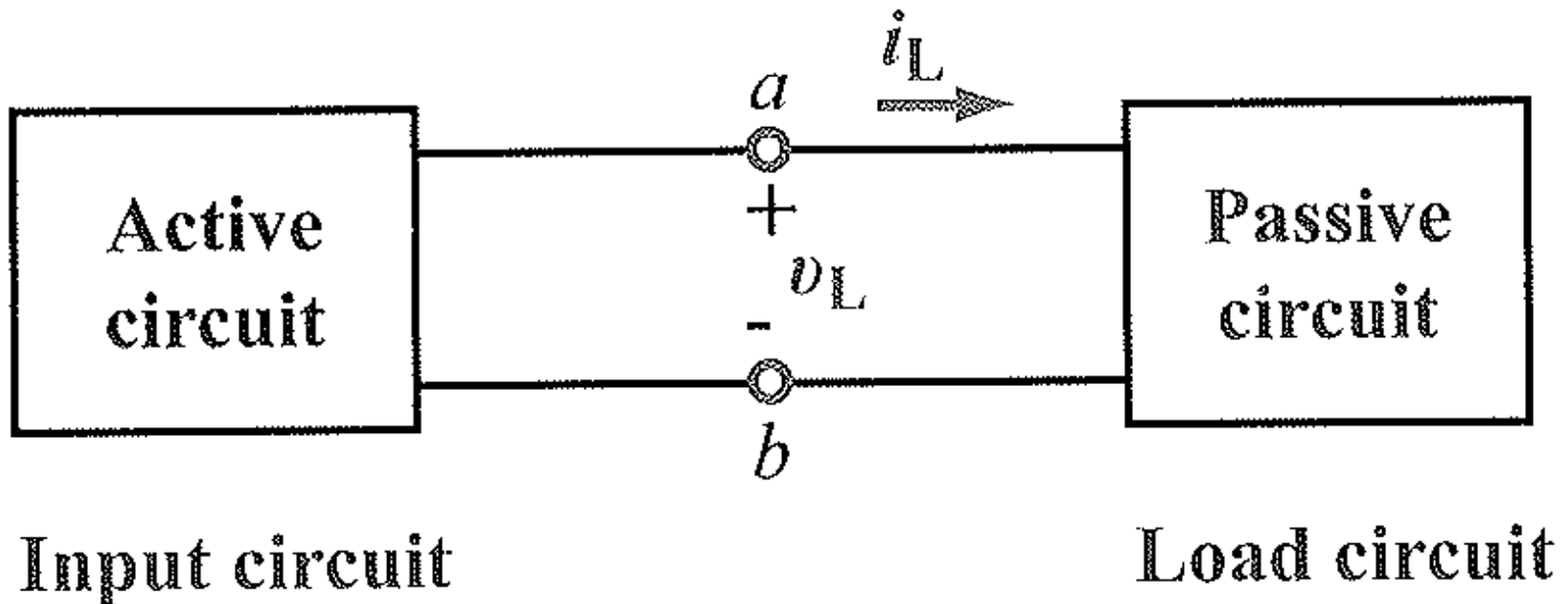


Maximizing Power Transfer in an Electric Circuit

Scott Starks, PhD, PE
Professor of ECE
UTEP

Model

- ▶ For certain applications, it is desirable to maximize the power (P_L) that is transferred from the Input circuit to the Load circuit.




Problem

- ▶ Given a specified Load circuit how does one approach the design of the load circuit to maximize the transfer of Power to the load?


Simplified Model

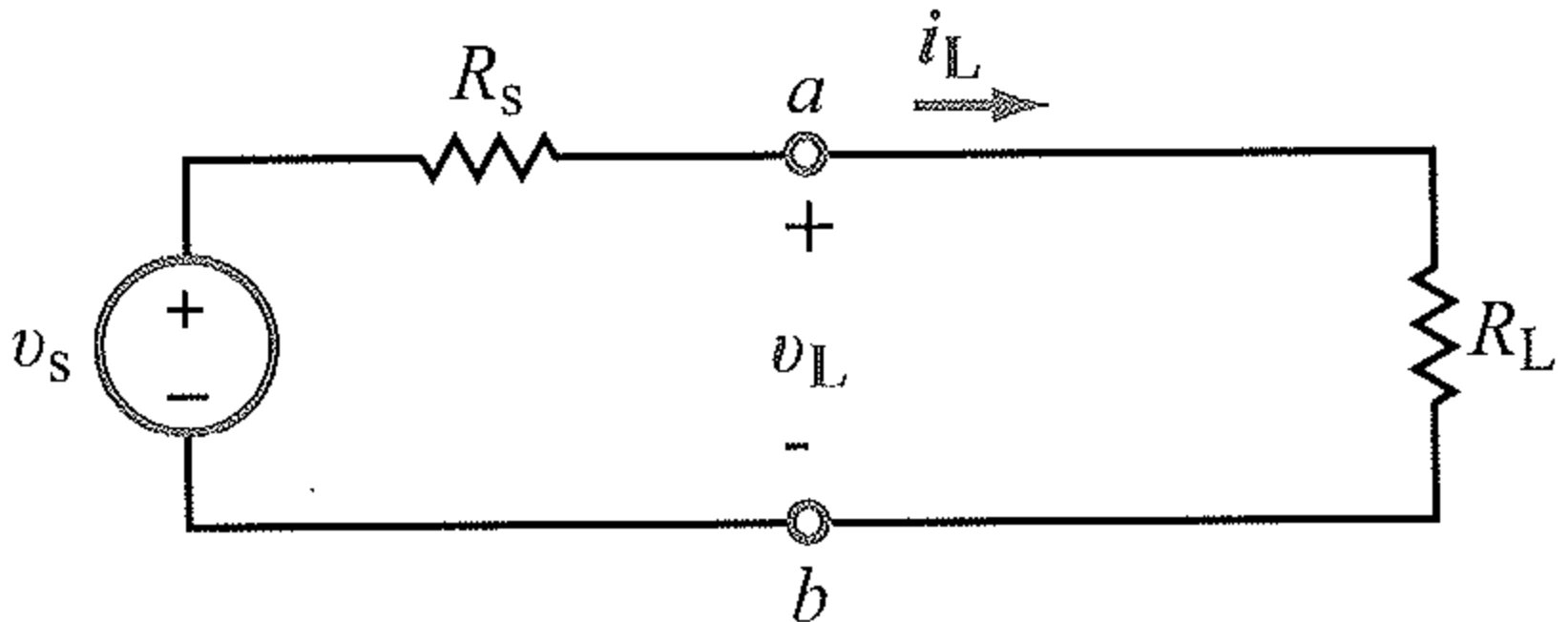- ▶ We begin by replacing the original Model with a Simplified Model.



Restatement of Problem (Based on Simplified Model)

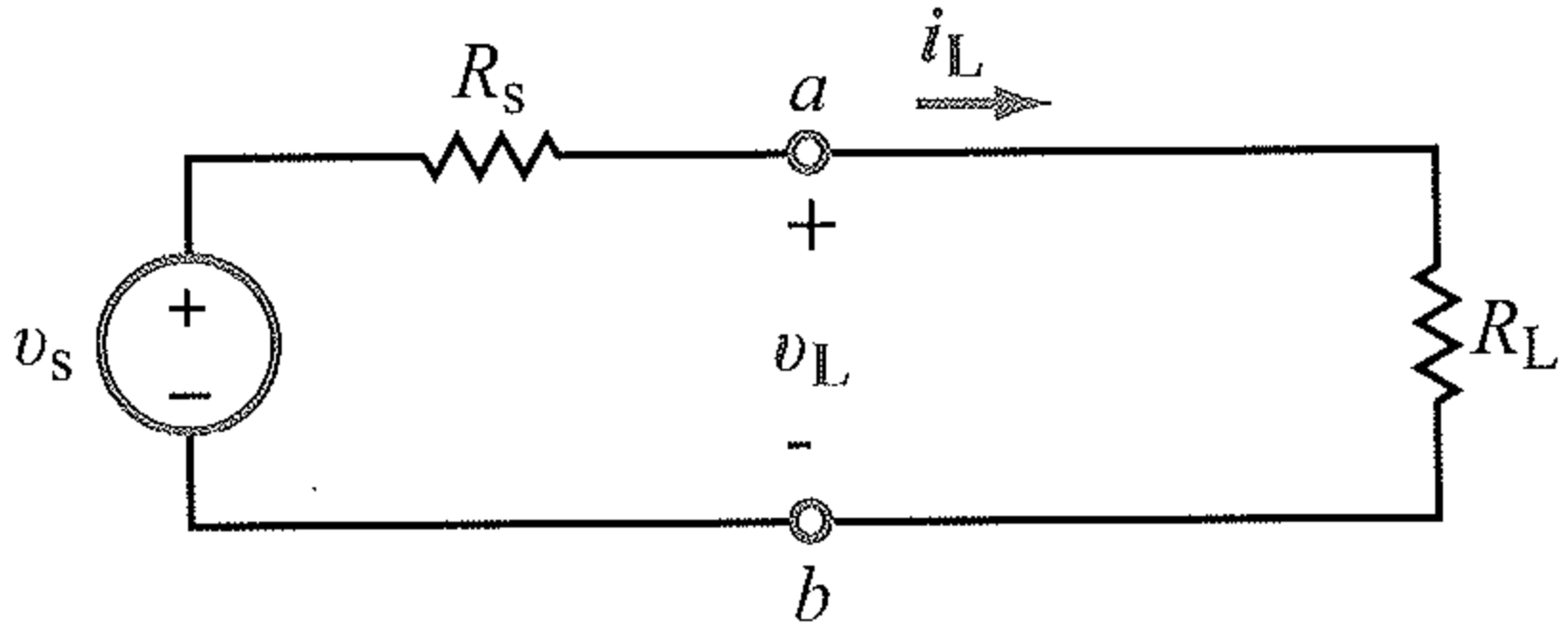- ▶ Find the value of R_L that achieves maximum Power transfer.




Analysis

- ▶ We first write expressions for the load current (i_L) and the load voltage (v_L).

$$i_L = \frac{v_s}{R_s + R_L}$$

$$v_L = \frac{v_s R_L}{R_s + R_L}$$

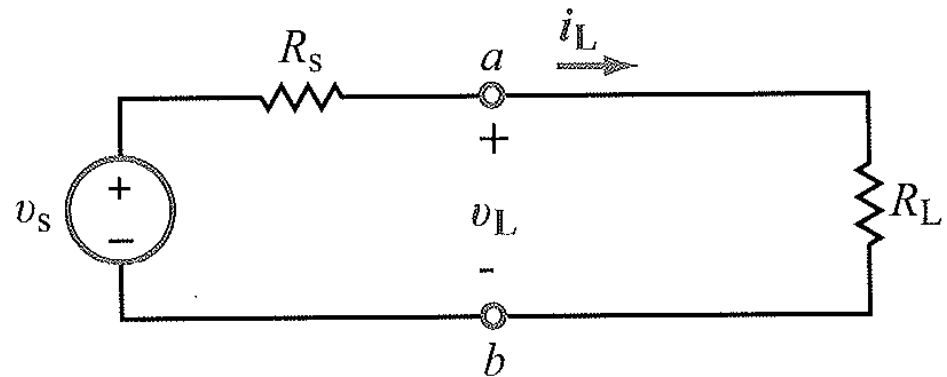


Power Transferred to the Load

- ▶ The power (P_L) that is transferred to the Load can be expressed as

$$P_L = i_L v_L = \frac{v_s R_L}{(R_s + R_L)^2}$$

Power as a Function of R_L

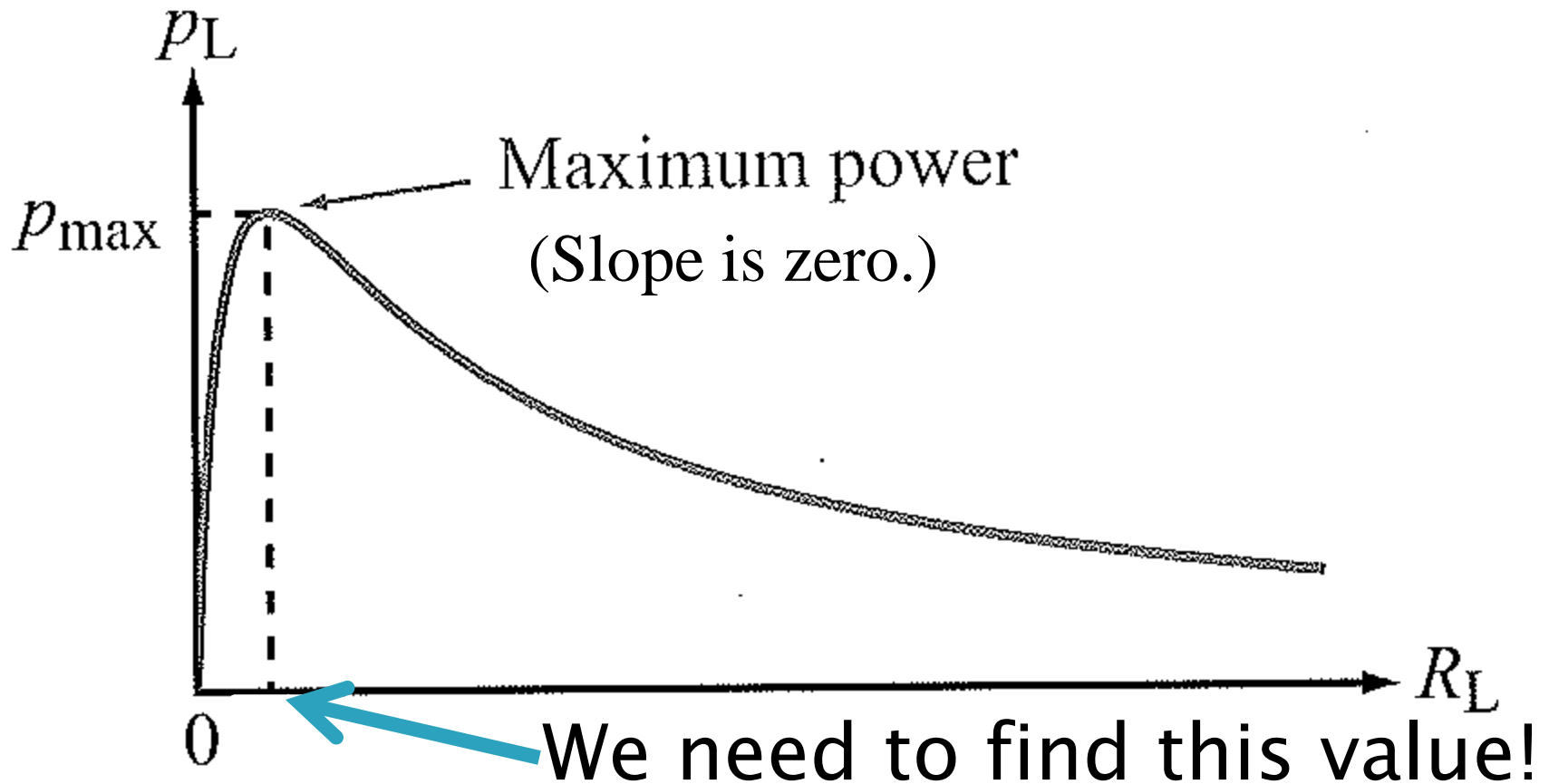- ▶ The expression for the Power transferred to the Load is a nonlinear function of R_L .



Derivative

- ▶ The derivative of P_L with respect to R_L is:

$$\frac{d P_L}{d R_L} = v_s \frac{(R_s + R_L)^2 - 2 R_L (R_s + R_L)}{(R_s + R_L)^4}$$

- ▶ The derivative is zero when the numerator is zero. Thus we must find the value for R_L that satisfies the equation:

$$(R_s + R_L)^2 - 2 R_L (R_s + R_L) = 0$$

$$(R_s + R_L)^2 - 2R_L(R_s + R_L) = 0$$

$$(R_s + R_L) - 2R_L = 0$$

$$(R_s + R_L) = 2R_L$$

$$R_s = R_L$$

So, maximum power is transferred to the load when the load has a resistance equal to the resistance of the source!

Summary

- ▶ The condition that should be met to achieve maximum power transfer is

$$R_L = R_s$$

- ▶ When this condition is met, the maximum power can be expressed as

$$P_{\max} = \frac{v_s^2 R_L}{(R_s + R_L)^2} = \frac{v_s^2}{4 R_L}$$